

# Useful Equations

The equations presented below are just a small selection taken from our detailed collection of high voltage Application Notes. The latest versions of these Application Notes can be downloaded from the TDK product center at <https://product.tdk.com/en/power/ale>. Currently available titles are;

- APP Note 500: Calculating Capacitor Charge Time**
- APP Note 502: Calculating AC Line Currents**
- APP Note 505: Charging units as Continuous Output DC Supplies**
- APP Note 507: Charging Large Load Capacitors**
- APP Note 509: What is Regulation and Repeatability?**
- APP Note 513: Power Factor Correction**
- APP Note 517: Protection Against Voltage Reversal**

## 1. Calculating Capacitor Charge Time

$$T_c = \frac{0.5 \times C_{load} \times V_{rated} \times V_{charge}}{P_{peak}}$$

- $T_c$  - time to charge load
- $C_{load}$  - load capacitance in Farads
- $V_{rated}$  - power supply rated output voltage in volts
- $V_{charge}$  - capacitor charge voltage in volts
- $P_{peak}$  - power supply peak charge rate in Joules per second

## 2. Average Power Rating Required

$$P_{av} = 0.5 \times C_{load} \times V_{rated} \times V_{charge} \times R$$

- $P_{av}$  - average power in watts
- $C_{load}$  - load capacitance in Farads
- $V_{rated}$  - power supply rated output voltage in volts
- $V_{charge}$  - capacitor charge voltage in volts
- $R$  - discharge repetition rate in Hz

## 3. AC line current draw

$$I_{1\phi} = \frac{P_{av}}{V_L \times PF \times Eff} \quad I_{3\phi} = \frac{P_{av}}{\sqrt{3} \times V_L \times PF \times Eff}$$

- $I_{1\phi}$  - single phase RMS line current
- $I_{3\phi}$  - three phase RMS line current per phase
- $P_{av}$  - average output power in watts
- $V_L$  - AC line voltage in volts
- $PF$  - Power Factor (see product data)
- $Eff$  - Efficiency (see product data)

## 4. Pulse to Pulse Repeatability

$$\delta V = \frac{1}{2 \times F_{switch} \times T_c}$$

- $\delta V$  - pulse to pulse repeatability (percentage)
- $T_c$  - time to charge load
- $F_{switch}$  - switching frequency of supply  
~ 40kHz for 500A, 102A, 152A, 202A, and LC1202  
~ 30kHz for 402, 802, 203, and 303

## 5. Continuous DC Operation

$$Ripple = \frac{I_{load}}{2 \times F_{switch} \times C_f}$$

- Ripple* - output voltage peak to peak ripple
- $I_{load}$  - current drawn by the load circuit
- $C_f$  - external filter capacitance across supply output
- $F_{switch}$  - switching frequency of supply  
~ 40kHz for 500A, 102A, 152A, 202A, and LC1202  
~ 30kHz for 402, 802, 203, and 303

## 6. Voltage Reversal Protection

Voltage reversal following load capacitor discharge can potentially damage the power supply. Any reverse current must be limited by a series resistor, or by a clamp diode and resistors to prevent the possibility of damage to the output diodes inside the supply. The degree of protection required is a function of reverse voltage, duration of reversal, and repetition rate of reversal. If the reverse current is greater than the rated current of the supply then a protection diode should be used.

Refer to our online Application Note 517 for details, and guidance in determining the protection component ratings.

