

App Note 517 - Voltage Reversal Protection

Simple Resistive Protection

When a high voltage is transmitted via a coaxial cable -such as the cable supplied with TDK-Lambda ALE HV Capacitor Charging Supplies- it should ideally be terminated in a resistance equal to or greater than the cable characteristic impedance. The resistor limits potential reflected energy from the shorted cable from reaching supply output stages. This reverse voltage can cause erratic operation, and potentially actual damage to the output section of the power supply. The sketch in figure 1 below shows a typical HV capacitor charging supply load connection.

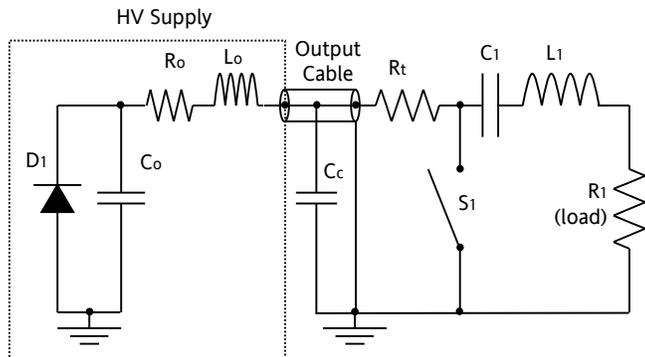


Figure 1. Generalized HV Supply Load Connection

If R_t is not in the circuit, when the switch S_1 closes the supply output cable (which is a short PFN) is discharged through S_1 along with the energy from C_1 . The pulse produced by discharging the output cable is inverted and reflected at the shorted switch S_1 and propagates back into the HV Supply output stages. The addition of R_t to the circuit presents a matched load to the supply output cable impedance, and hence the pulse produced when S_1 is closed is dissipated in R_t .

The value of R_t is typically 50 to 500 Ω with a power rating of 200W. This rating ensures enough physical size to provide sufficient voltage holdoff capability during the discharge period. For example, the power rating of the terminating resistor for a series 303 supply @ 40kV can be calculated as follows:

$$I_{out} = 1.88A, R_t = 50W$$

$$\text{Average power is } = 1.88^2 \times 50 = 177 \text{ Watts}$$

There are two additional sources of current that can cause the dissipated power to increase by several orders of magnitude. The first source is the distributed energy stored in the supply output cable capacitance C_c . With reference to figure 1, the internal capacitance of the supply C_o along with C_c is discharged through R_t and R_o (R_o represents the supply output resistance which is typically a few ohms or less) every time S_1 closes.

A typical value for C_o can be 200pF, and C_c is related to the length of output cable (~30pF/ft) which could be 300pF for a standard 10ft cable.

Assuming a circuit charge voltage of 40kV the stored energy in C_o and C_c can simply be calculated using the following equation;

$$E = \frac{1}{2}CV^2 = \frac{1}{2} \times (500pF) \times (40kV)^2 = 0.4 \text{ Joules}$$

If the discharge circuit is operating at a repetition rate (rep. rate) of 1kHz, then the mean power dissipated in R_t and R_o is 0.4 Joules x 1000 or 400W.

Additional power dissipation in R_t may be caused by voltage reversal across due to an underdamped discharge. For example in a positive output power supply, if the discharge circuit is underdamped when switch S_1 closes the voltage on the HV cable will undershoot and a transient negative voltage is applied to the supply output stage. When this occurs current will flow out of the power supply through the now forward biased output rectifiers and R_t to ground. This is illustrated in Figure 2 below.

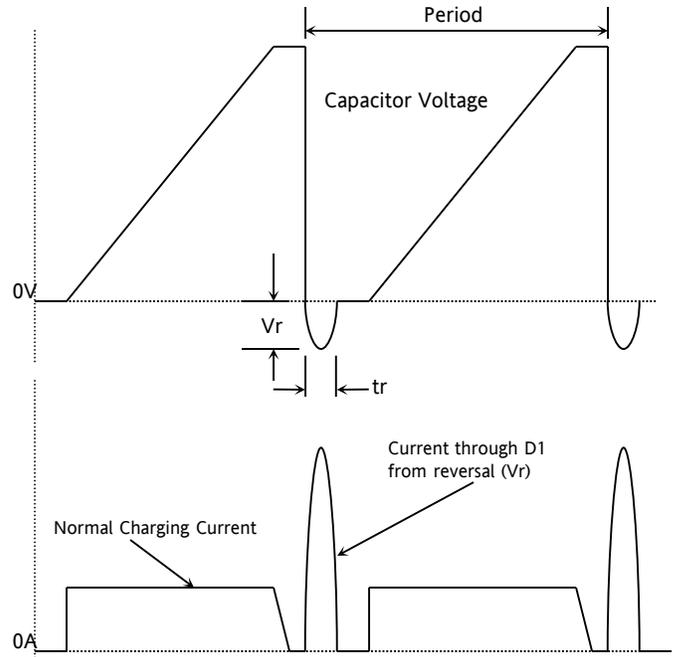


Figure 2. HV Supply output diode current under voltage reversal conditions.

If the peak current associated with load voltage reversal is large enough, damage to the output rectifiers may occur. The damage threshold for voltage reversal is difficult to quantify but if a reversal causes the output current to be greater than the supply rated output current then a protection diode should be added to the load circuit.

The following formula can be used as a guide when deciding whether or not to include a reverse protection diode.

$$\text{Diode required if: } \frac{V_r}{R_t} > I_{rated}$$

Where; V_r is the voltage reversal in volts,
 I_{rated} is rated output current of the HV supply
 R_t is series resistance shown in Figure 1

App Note 517 - Voltage Reversal Protection (continued)

Diode Resistor Protection

A typical load circuit with an additional protection diode is shown in Figure 3 below.

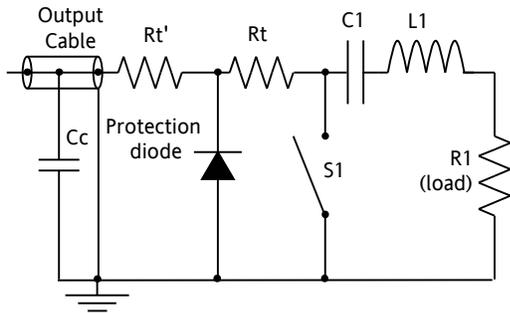


Figure 3. Voltage Reversal Protection Circuit

The choice of protection diode is very important to achieve reliable and effective reversal protection. The user must ensure that the following three diode ratings are sufficient for the application.

- The **diode reverse voltage** rating must be greater than the circuit operating voltage, and the supply operating voltage.
- The **RMS. current** through the diode is less than the manufacturers rated figure.
- The **forward voltage drop** across the diode during conduction should be less than the voltage drop across the diodes in the supply if Rt' is not used.

For safety sake the user should factor the diode rated voltage by approx. 1.5 to give a margin in case any overvoltage transients are present in the load circuit. In the case of a 20kV supply the reverse protection diode should be rated at approximately 30kV.

The protection diode RMS. current rating must be greater than the current due to load voltage reversals. The RMS. rating can be determined using the following steps.

Peak current through the protection diode during voltage reversal is determined from;

$$I_{pk} = \frac{V_r}{R_t}$$

Where R_t is the resistor shown in the circuit of figure 3. For pulse reversal the RMS. current during a single cycle is;

$$I_{rms} (pulse) = \frac{I_{pk}}{\sqrt{2}}$$

With repetitive load operation the overall RMS. current in the protection diode can be determined from RMS. current for a single cycle and the duty cycle of the reversal event, as below;

$$I_{rms} = I_{rms} (pulse) \times \sqrt{duty\ cycle}$$

V_r can be measured on a scope using an HV probe, or for the worst case assume $V_r = V_{charge}$. To measure V_r , start with the power supply set to a low output voltage without a bypass diode for the first measurements and calculate the percent reversal. Use this as a guide as what to expect at full voltage, thus avoiding operation at full voltage without a bypass diode.

Knowing the forward voltage drop across the protection diode is critical in achieving effective supply protection. The circuit in figure 4 shows the equivalent supply output circuit with a voltage reversal.

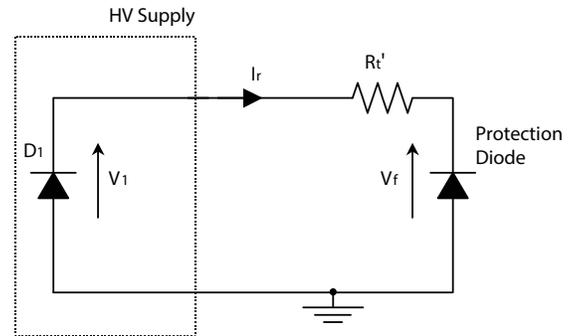


Figure 4. Supply equivalent output circuit with reverse protection diode shown.

The reverse current I_r is given from;

$$I_r = \frac{V_f - V_1}{R_t'}$$

The resistance of R_t' should be selected to maintain I_r at a figure less than or equal to the supply rated output current. The key figure in selecting the protection diode is to ensure that V_f is as low as possible. If $V_f < V_1$, then R_t' may not be necessary.

The critical parameters which should be considered when selecting the reverse protection diode are;

Reverse Voltage Rating - Should be greater than supply operating voltage.

RMS. Current Rating - should be greater than I_{rms} due to load voltage reversal.

Forward Voltage Drop - as small as possible.

Note: The recovery time of the voltage reversal protection diode does not have to be fast.

High Voltage Diode manufacturers

Semtech - Newbury Park, CA. 91320. Tel. 800-298-2111.
Web: www.semtech.com

Dean Technology, Inc. - Dallas, TX. Tel. 972-248-7691
Web: www.deantechnology.com

VMI - Visalia, CA. Tel. 209-651-1402.
Web: www.voltagemultipliers.com

If you have any questions or comments regarding this or any of our Application Notes or products, please contact Andy Tydeman at the factory, we are here to help.

Information cannot be guaranteed and may be subject to change without notice.